

Lab: AC Problems 2

Name _____ Period _____

Rounding off to one significant digit,

- a. **Diagram** a series circuit with a 3 henry coil, a 0.00002 farad capacitor, and a 1000 ohm resistor powered by a 150 volt 60 Hz generator.
- b. find the inductive reactance, X_L . (ans. 1000 ohms)
- c. the capacitive reactance, X_C . (ans. 100 ohms)
- d. **sketch** the vector diagram and label it with X_L , X_C , and R.
- e. solve for the impedance, Z. (ans. 1300 ohms, round to 1000 ohms)
- f. find the amperage, I. (ans 0.2 a)
- g. find the resonant frequency, f. (ans. 20 Hz)
- h. find the phase angle, θ . (ans. 40°)
- i. find the power, P. (ans. 20 watts)

CRITIQUE: