

Lab: Three Way Switch Circuit

Name _____ Period _____

PURPOSE: To design, draw, and test a circuit by which two switches will control one light.

PROCEDURE: Design *on paper first* a three way circuit. Using Two Single Pole, Double Throw Switches, a battery, and a light, test it and **have it checked off by The Boom**. Beware! If your switches are double poled, **use only ONE side of it**.

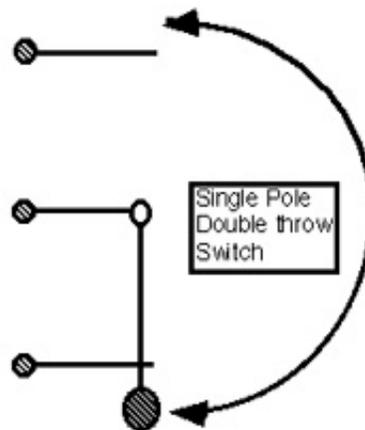
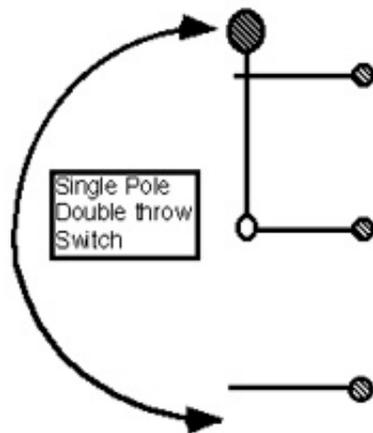
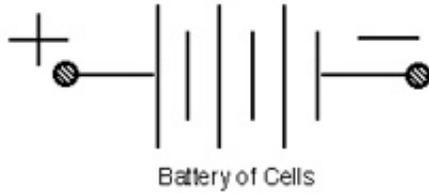
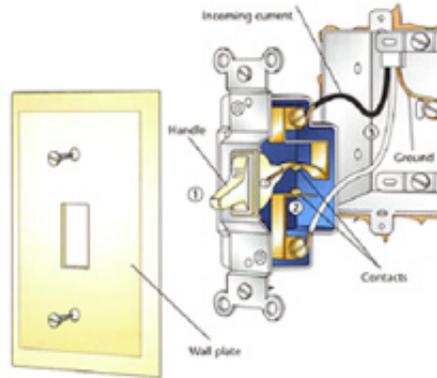


Diagram and Critique on back: